

Aung Kyi San
Summer 2012

ECE 20200 : Linear Circuit Analysis II
School of ECE, Purdue University

LECTURE 14

- Frequency Response $H(j\omega)$

Reference :

Decarlo/Lin


pp 707-714

FREQUENCY RESPONSE OF SIMPLE CIRCUITS

Ray DeCarlo
School of ECE
Purdue University
West Lafayette, IN 47907-1285
decarlo@ecn.purdue.edu

I. WHAT IS FREQUENCY RESPONSE?

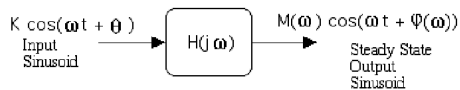1. Recall Sinusoidal Steady State Analysis



- (a) $M(\omega) = K \times |H(j\omega)|$ -- ω -dependent gain
(b) $\phi(\omega) = \angle H(j\omega) + \theta$ -- ω -dependent phase

2. DEFINITION: the **frequency response** of a circuit/system is $H(j\omega) = H(s)|_{s=j\omega}$, i.e., $H(s)$ evaluated along the imaginary axis.


NOTE: for each ω , $H(j\omega)$ is a complex number:

$$H(j\omega) \Leftrightarrow |H(j\omega)| \angle H(j\omega)$$

- (a) $\angle H(j\omega)$ is the **phase response**, and
(b) $|H(j\omega)|$ is the **magnitude response/GAIN**.


EXAMPLE 1. Plot the Phase and Magnitude of $H(s) = \frac{s+10}{s+400}$.

$s = j\omega$	$j0$	$j\infty$	$j10$	$j400$
$ H(j\omega) $	0.025	1	$\frac{10\sqrt{2}}{\sqrt{10^2+400^2}} = \frac{10\sqrt{2}}{400}$	$\frac{400}{400\sqrt{2}} = \frac{1}{\sqrt{2}}$
$\angle H(j\omega)$	0	0	$\angle \frac{10+j10}{400+j10} = 45^\circ - 0 = 45^\circ$	$\angle \frac{10+j400}{400+j400} = 90^\circ - 45^\circ = 45^\circ$

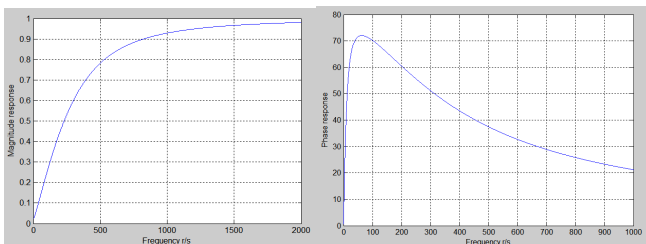

```
n = [1 10]; % numerator coefficients
d = [1 400]; % denom coefficients
w = 0.1:0.1:2000; % Frequency range
h = freqs(n,d,w); % Freq response calculation
figure(1); plot(w,abs(h)); grid; xlabel('Frequency r/s'); ylabel('Magnitude response')
figure(2); plot(w,angle(h)*180/pi); grid; xlabel('Frequency r/s'); ylabel('Phase response')
```

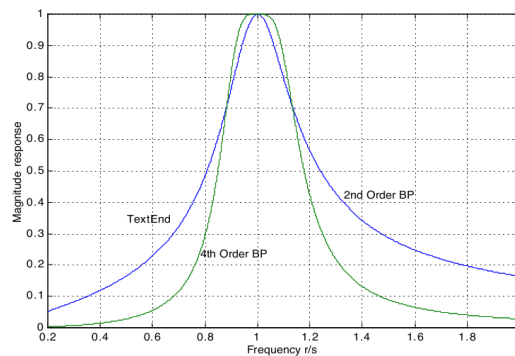EXAMPLE 2. A **band pass (BP)** transfer function is one that passes frequencies in a (narrow) frequency band and eliminates/attenuates-significantly those freqs outside the band.



(i) 2nd order **BP** transfer function (blue curve):

$$H_1(s) = \frac{0.25s}{s^2 + 0.25s + 1} = \frac{0.25s}{(s + 0.125)^2 + (0.992)^2}$$

(ii) 4th order **BP** transfer function (green curve):

$$H_2(s) = \frac{0.0625s^2}{s^4 + 0.35355s^3 + 2.0625s^2 + 0.35355s + 1}$$

$$= \frac{\sqrt{0.0625}s}{(s + 0.0962)^2 + (1.0884)^2} \times \frac{\sqrt{0.0625}s}{(s + 0.08058)^2 + (0.91164)^2}$$

Remark: $s = j\omega = 0$ and $s = j\omega = \infty$ are the two most important frequencies:

- (a) $H_1(0) = H_1(j\infty) = 0$ (magnitude is zero at dc and infinity)
(b) $H_2(0) = H_2(j\infty) = 0$



(iii) Plot $|H(j\omega)|$ using the following MATLAB code:

```
>n1 = 0.25*[1 0]; % numerator coefficients H1
>d1 = [1 0.25 1]; % denom coefficients H2
>n2 = 0.0625*[1 0 0]; % numerator coefficients H2
>d2 = [1 3.5355e-01 2.0625 3.5355e-01 1];
>w=0.2:0.005:2; % Frequency range
>h1 = freqs(n1,d1,w); % Freq response calculation
>h2 = freqs(n2,d2,w);
>plot(w,abs(h1),w,abs(h2))
>grid
>xlabel('Frequency r/s')
>ylabel('Magnitude response')
>gtext('2nd Order BP')
>gtext('4th Order BP')
```

Aung Kyi San Summer 2012

ECE 20200 : Linear Circuit Analysis II School of ECE, Purdue University

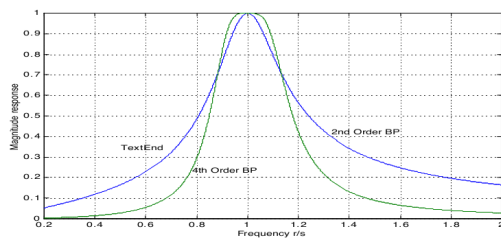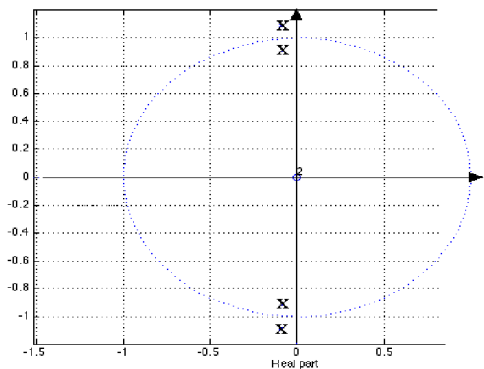(b) Qualitative Analysis Using Pole-zero plot. Imagine, as you walk along the imaginary axis, what happens to your height as you near a pole, a double pole, and then as you near a zero.




(c) The Idea of Frequency Scaling:

```


»Kf = 1000; % Frequency Scale Factor
»n1 = 0.25*[1/Kf 0]; % s → s/Kf in num coefficients of H1
»d1 = [1/Kf^2 0.25/Kf 1]; % s → s/Kf in denom coefficients of H1
»n2 = 0.0625*[1/Kf^2 0 0]; % s → s/Kf in num coefficients of H2
»d2 = [1/Kf^4 3.5355e-01/Kf^3 2.0625/Kf^2 3.5355e-01/Kf 1];
»w=0.2*Kf:1:2*Kf; % Freq range is scaled up proportionately
»h1 = freqs(n1,d1,w);
»h2 = freqs(n2,d2,w);
»plot(w,abs(h1),w,abs(h2))
»grid
»xlabel('Frequency r/s')
»ylabel('Magnitude response')
»gtext('2nd Order BP')
»gtext('4th Order BP')

```

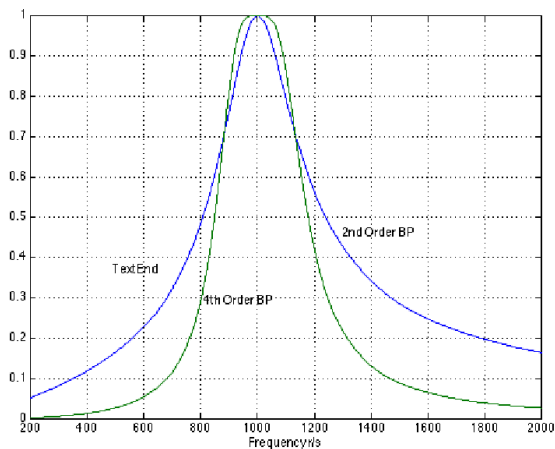


EXAMPLE 3. Magnitude response $|H(j\omega)|$ of three (so called) normalized low pass (LP) Butterworth filter transfer functions:

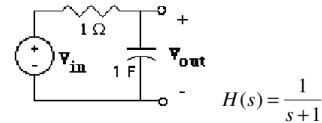(a) First Order Normalized LP Butterworth



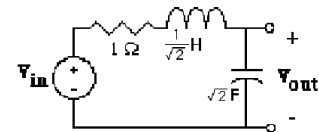
(b) 2nd Order Normalized Butterworth (how many ∞ zeros)

$$H(s) = \frac{1}{s^2 + \frac{R_s}{L}s + \frac{1}{LC}} = \frac{1}{s^2 + \sqrt{2}s + 1}$$



(c) 3rd Order Normalized Butterworth (how many ∞ zeros)

$$H(s) = \frac{1}{s^3 + 2s^2 + 2s + 1}$$

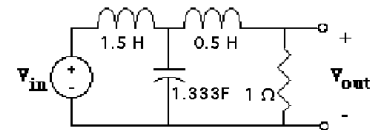


(d) MATLAB Code for frequency response calculation given H(s):

```

»w = logspace(-2,2,800);
»n1 = 1; d1 = [1 1];
»n2 = 1; d2 = [sqrt(2) 1];
»n3 = 1; d3 = [1 2 2 1];
»h1 = freqs(n1,d1,w);
»h2 = freqs(n2,d2,w);
»h3 = freqs(n3,d3,w);
»semilogx(w,abs(h1),w,abs(h2),w,abs(h3))
»grid
»xlabel('Normalized rad frequency')
»ylabel('Magnitude Response')

```

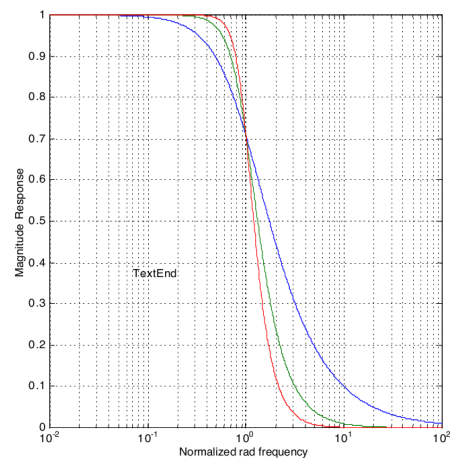
(e) Magnitude Response Plots (Note transitions of gain from 1 to near 0)



Aung Kyi San Summer 2012

ECE 20200 : Linear Circuit Analysis II School of ECE, Purdue University

(f) Pole-Zero Plot of 2nd and 3rd Order (Normalized) Butterworth Filters—Notes: How many infinite zeros? Poles lie on the unit circle in left half complex plane. Are such filters stable??

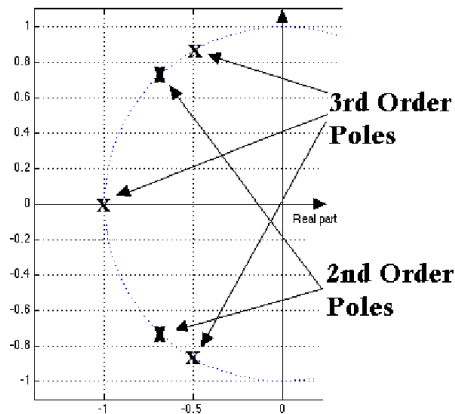


EXAMPLE 4. Plot of $|H(j\omega)|$ of three low pass Butterworth transfer functions of frequency scaled by $K_f = 1000$:

$$H_{new}(s) = H_{old}\left(\frac{s}{K_f}\right) = \frac{1}{\left(\frac{s}{1000}\right) + 1}$$

$$H_{new}(s) = H_{old}\left(\frac{s}{K_f}\right) = \frac{1}{\left(\frac{s}{1000}\right)^2 + \sqrt{2}\left(\frac{s}{1000}\right) + 1}$$

$$H_{new}(s) = H_{old}\left(\frac{s}{K_f}\right) = \frac{1}{\left(\frac{s}{1000}\right)^3 + 2\left(\frac{s}{1000}\right)^2 + 2\left(\frac{s}{1000}\right) + 1}$$


Note: Same Plots as before with cut-off frequency at 1000.

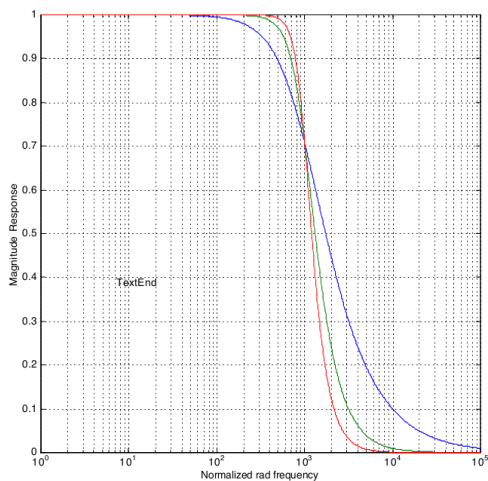

EXAMPLE 5. Frequency response of the (**High Pass-HP**) RC circuit; Capacitor has high impedance for low frequencies and low impedance for high frequencies.

(a) Transfer function: $H(s) = \frac{s}{s + \frac{1}{C}} = \frac{s}{s + 100}$ by V-division.

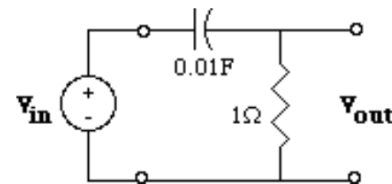(i) One pole at $s = -100$; one zero at $s = 0$.



$$(b) \quad s = j\omega, \quad H(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega CR}{j\omega CR + 1} = \frac{j\frac{\omega}{100}}{j\frac{\omega}{100} + 1}$$


STEP 2. ASYMPTOTIC BEHAVIOR: IMPORTANT FREQUENCIES ARE:

0, ∞, AND ????

$\omega \rightarrow \infty$	$ H(j\omega) = \left \frac{R}{R + \frac{1}{j\omega C}} \right \rightarrow 1$	$\angle H(j\omega) \rightarrow 0$
$\omega \rightarrow 0$	$ H(j\omega) = \left \frac{j\omega CR}{j\omega CR + 1} \right \rightarrow 0$	$\angle H(j\omega) \rightarrow 90^\circ$
$\omega \rightarrow 100$	$ H(j\omega) = \left \frac{j\frac{\omega}{100}}{j\frac{\omega}{100} + 1} \right \rightarrow \frac{1}{\sqrt{2}}$	$\angle H(j\omega) \rightarrow 45^\circ$

STEP 3. PLOTS FROM MATLAB:
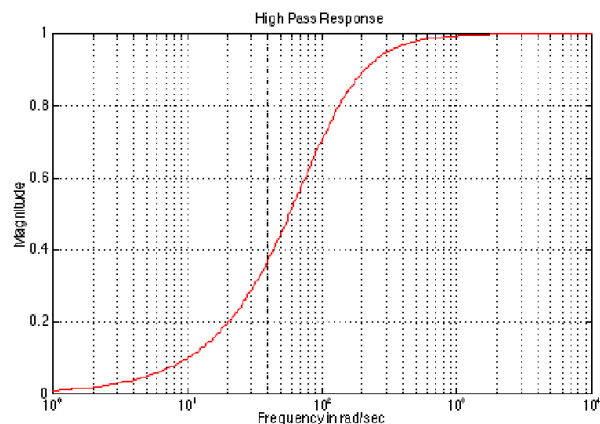
```
>w = logspace(0,4,500);
>H = freqs([1 0],[1 100],w);
>semilogx(w,abs(H))
>grid
>xlabel('Frequency in rad/sec')
>ylabel('Magnitude')
>>
```




Aung Kyi San Summer 2012


```

»semilogx(w,180*angle(H)/pi)
»grid
»xlabel('Frequency rad/sec')
»ylabel('Angle in degrees')

```

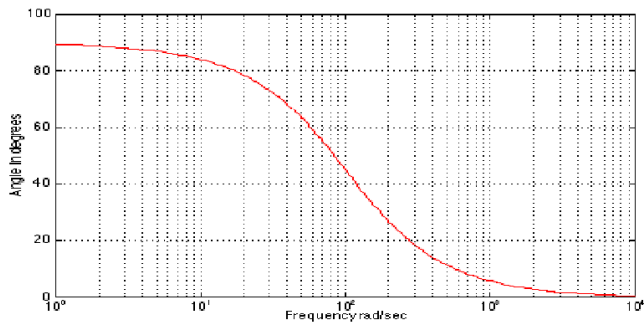

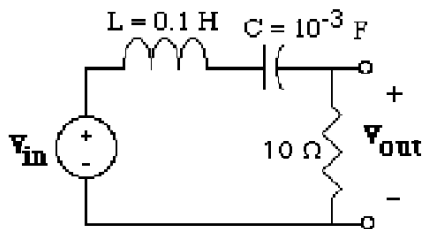EXAMPLE 6. Frequency response of the (Band Pass-BP) RLC circuit



STEP 1: CALCULATION OF TRANSFER FUNCTION: By V-division,

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R}{R + Ls + \frac{1}{Cs}} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

NOTE: a finite zero at $s = 0$ and one infinite zero;
two finite poles at $s = -50 \pm j86.6$

ECE 20200 : Linear Circuit Analysis II School of ECE, Purdue University

STEP 2: IMPORTANT FREQUENCIES AND ASYMPTOTIC BEHAVIOR

ω (rad/sec)	$H(j\omega) = \frac{j\frac{\omega}{L}}{\frac{1}{LC} - \omega^2 + j\frac{\omega}{L}} = \frac{j10\omega}{10^4 - \omega^2 + j10\omega}$
$\omega \rightarrow 0$	$ H(j\omega) \angle H(j\omega) \rightarrow 0 \angle 90^\circ$
$\omega \rightarrow \infty$	$ H(j\omega) \angle H(j\omega) \rightarrow 0 \angle 0^\circ$
$\omega \rightarrow 100$	$ H(j\omega) \angle H(j\omega) \rightarrow 1 \angle 0^\circ$
??	$ H(j\omega) \angle H(j\omega) \rightarrow \frac{1}{\sqrt{2}} \angle 45^\circ$
??	$ H(j\omega) \angle H(j\omega) \rightarrow \frac{1}{\sqrt{2}} \angle -45^\circ$


Hint: for what values of ω are the magnitudes of the real and imaginary parts of the denominator equal?

STEP 3. PLOTS FROM MATLAB:

```

w = logspace(0.4,1.000);
R = 10; L = 0.1; C = 1e-3;
n = [R/L 0];
d = [1 R/L 1/(L*C)];
h = freqs(n,d,w);
semilogx(w,abs(h))
grid
xlabel('Frequency in rad/s')
ylabel('Magnitude Response')

```

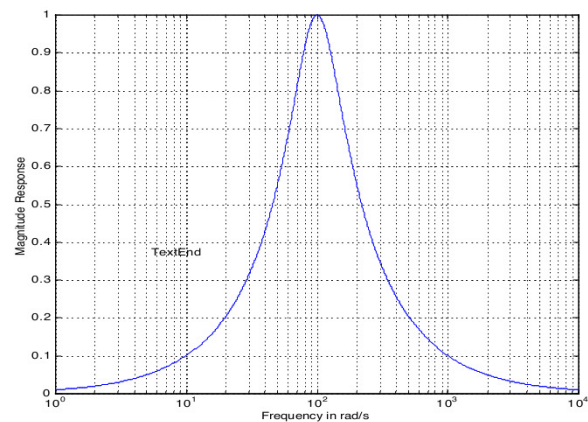


NOTE: a finite zero at $s = 0$ and one infinite zero;
two finite poles at $s = -50 \pm j86.6$

Aung Kyi San Summer 2012


```

»semilogx(w,angle(h)*180/pi)
»grid
»xlabel('Frequency in rad/s')
»ylabel('Phase Response')



```

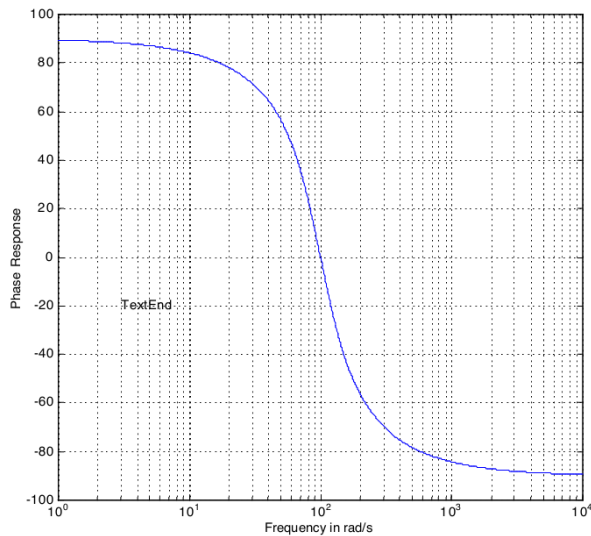

ECE 20200 : Linear Circuit Analysis II School of ECE, Purdue University

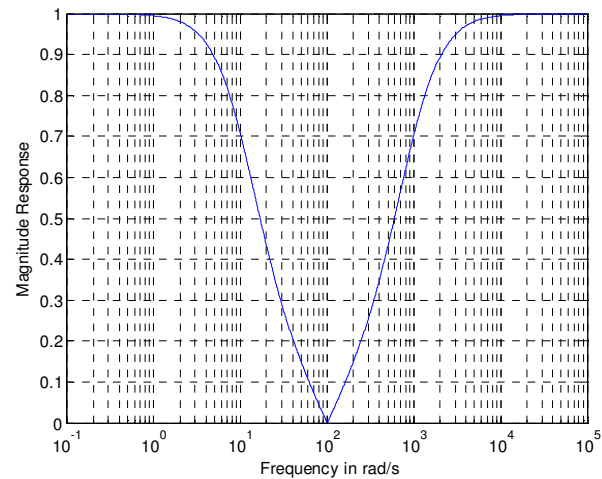

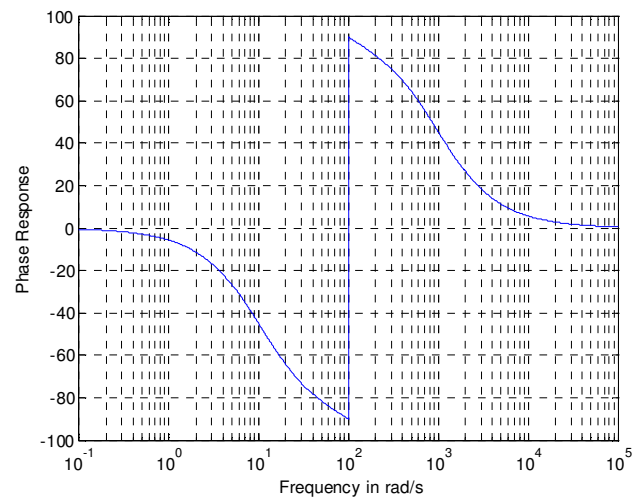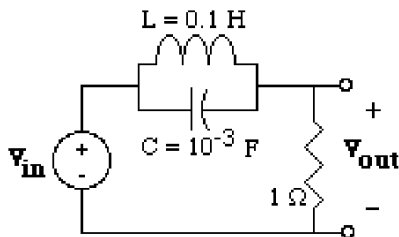EXAMPLE 7. Frequency response of the (**Band Reject-BR**) RLC circuit: Passes most frequencies with little or no attenuation and rejects a small band of frequencies.



STEP 1: CALCULATION OF TRANSFER FUNCTION: By V-division,

$$H(s) = \frac{R}{R + \frac{1}{Cs + \frac{1}{Ls}}} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Remark: Zeros at $\frac{\pm j}{\sqrt{LC}} = \pm j100$, frequencies around $\pm j100$ are

mostly gone:
$$H(j\omega) = \frac{\frac{1}{LC} - \omega^2}{\frac{1}{LC} - \omega^2 + \frac{j\omega}{RC}}$$

```

w = logspace(-1,5,1000);
R = 1; L = 0.1; C = 1e-3;
n = [1 0 1/(L*C)];
d = [1 1/(R*C) 1/(L*C)];
h = freqs(n,d,w);
figure(1)
semilogx(w,abs(h))
grid
xlabel('Frequency in rad/s')
ylabel('Magnitude Response')
figure(2)
semilogx(w,angle(h)*180/pi)
grid
xlabel('Frequency in rad/s')
ylabel('Phase Response')

```